# Optimizing S-box Implementations for Several Criteria using SAT Solvers



Provably minimal implementations of small functions with respect to:

• Multiplicative complexity Minimize nonlinear operations (masking, MPC, FHE)





Provably minimal implementations of small functions with respect to:

- Multiplicative complexity Minimize nonlinear operations (masking, MPC, FHE)
- Bitslice gate complexity Use only AND, OR, XOR, NOT (bitsliced software)



Provably minimal implementations of small functions with respect to:

- Multiplicative complexity Minimize nonlinear operations (masking, MPC, FHE)
- Bitslice gate complexity Use only AND, OR, XOR, NOT (bitsliced software)
- Gate complexity

Also use NAND, NOR, XNOR (hardware, area)





Provably minimal implementations of small functions with respect to:

- Multiplicative complexity
  - Minimize nonlinear operations (masking, MPC, FHE)
- Bitslice gate complexity Use only AND, OR, XOR, NOT (bitsliced software)
- Gate complexity

Also use NAND, NOR, XNOR (hardware, area)

• Circuit depth complexity

Trade-off #gates and depth (hardware, latency)



Provably minimal implementations of small functions with respect to:

- Multiplicative complexity
  - Minimize nonlinear operations (masking, MPC, FHE)
- Bitslice gate complexity Use only AND, OR, XOR, NOT (bitsliced software)
- Gate complexity

Also use NAND, NOR, XNOR (hardware, area)

• Circuit depth complexity

Trade-off #gates and depth (hardware, latency)



Provably minimal implementations of small functions with respect to:

- Multiplicative complexity
  - Minimize nonlinear operations (masking, MPC, FHE)
- Bitslice gate complexity Use only AND, OR, XOR, NOT (bitsliced software)
- Gate complexity

Also use NAND, NOR, XNOR (hardware, area)

• Circuit depth complexity

Trade-off #gates and depth (hardware, latency)

Generic solution: encode as SAT instance, solve, retrieve implementation



# Encoding the MCDP

Multiplicative Complexity Decision Problem

Given a function f and some positive integer k, is there a circuit that implements f and that uses at most k nonlinear operations?





# Encoding the MCDP

Multiplicative Complexity Decision Problem

Given a function f and some positive integer k, is there a circuit that implements f and that uses at most k nonlinear operations?

Encoding by Courtois, Mourouzis, and Hulme [CMH13, Mou15]

- Let x<sub>i</sub> be variables representing S-box inputs
- Let y<sub>i</sub> be variables representing S-box outputs
- Let q<sub>i</sub> be variables representing gate inputs
- Let *t<sub>i</sub>* be variables representing gate outputs
- Let *a<sub>i</sub>* be variables representing wiring between gates



# Encoding the MCDP

Multiplicative Complexity Decision Problem

Given a function f and some positive integer k, is there a circuit that implements f and that uses at most k nonlinear operations?

Encoding by Courtois, Mourouzis, and Hulme [CMH13, Mou15]

- Let x<sub>i</sub> be variables representing S-box inputs
- Let y<sub>i</sub> be variables representing S-box outputs
- Let q<sub>i</sub> be variables representing gate inputs
- Let t<sub>i</sub> be variables representing gate outputs
- Let *a<sub>i</sub>* be variables representing wiring between gates

For example, lets encode a 4x4 S-box with k = 3



$$\begin{aligned} q_0 &= a_0 + a_1 \cdot x_0 + a_2 \cdot x_1 + a_3 \cdot x_2 + a_4 \cdot x_3 \\ q_1 &= a_5 + a_6 \cdot x_0 + a_7 \cdot x_1 + a_8 \cdot x_2 + a_9 \cdot x_3 \\ t_0 &= q_0 \cdot q_1 \\ q_2 &= a_{10} + a_{11} \cdot x_0 + a_{12} \cdot x_1 + a_{13} \cdot x_2 + a_{14} \cdot x_3 + a_{15} \cdot t_0 \\ q_3 &= a_{16} + a_{17} \cdot x_0 + a_{18} \cdot x_1 + a_{19} \cdot x_2 + a_{20} \cdot x_3 + a_{21} \cdot t_0 \\ t_1 &= q_2 \cdot q_3 \\ q_4 &= a_{22} + a_{23} \cdot x_0 + a_{24} \cdot x_1 + a_{25} \cdot x_2 + a_{26} \cdot x_3 + a_{27} \cdot t_0 + a_{28} \cdot t_1 \\ q_5 &= a_{29} + a_{30} \cdot x_0 + a_{31} \cdot x_1 + a_{32} \cdot x_2 + a_{33} \cdot x_3 + a_{34} \cdot t_0 + a_{35} \cdot t_1 \\ t_2 &= q_4 \cdot q_5 \\ y_0 &= a_{36} \cdot x_0 + a_{37} \cdot x_1 + a_{38} \cdot x_2 + a_{39} \cdot x_3 + a_{40} \cdot t_0 + a_{41} \cdot t_1 + a_{42} \cdot t_2 \\ y_1 &= a_{43} \cdot x_0 + a_{44} \cdot x_1 + a_{45} \cdot x_2 + a_{46} \cdot x_3 + a_{47} \cdot t_0 + a_{48} \cdot t_1 + a_{49} \cdot t_2 \\ y_2 &= a_{50} \cdot x_0 + a_{51} \cdot x_1 + a_{59} \cdot x_2 + a_{50} \cdot x_3 + a_{61} \cdot t_0 + a_{57} \cdot t_1 + a_{56} \cdot t_2 \\ y_3 &= a_{57} \cdot x_0 + a_{58} \cdot x_1 + a_{59} \cdot x_2 + a_{60} \cdot x_3 + a_{61} \cdot t_0 + a_{62} \cdot t_1 + a_{63} \cdot t_2 \end{aligned}$$





Not bound to specific S-box yet

• Consider S-box as lookup table with  $2^n$  entries (x, y)



- Consider S-box as lookup table with  $2^n$  entries (x, y)
- A correct circuit works for all possible values



- Consider S-box as lookup table with  $2^n$  entries (x, y)
- A correct circuit works for all possible values
- Create 2<sup>n</sup> copies of equations Note: unfortunately this encoding grows exponentially



- Consider S-box as lookup table with  $2^n$  entries (x, y)
- A correct circuit works for all possible values
- Create 2<sup>n</sup> copies of equations Note: unfortunately this encoding grows exponentially
- Rename  $x_i$ ,  $y_i$ ,  $q_i$ ,  $t_i$ , but not  $a_i$



- Consider S-box as lookup table with  $2^n$  entries (x, y)
- A correct circuit works for all possible values
- Create 2<sup>n</sup> copies of equations Note: unfortunately this encoding grows exponentially
- Rename  $x_i$ ,  $y_i$ ,  $q_i$ ,  $t_i$ , but not  $a_i$
- Concatenate



- Consider S-box as lookup table with  $2^n$  entries (x, y)
- A correct circuit works for all possible values
- Create 2<sup>n</sup> copies of equations Note: unfortunately this encoding grows exponentially
- Rename  $x_i$ ,  $y_i$ ,  $q_i$ ,  $t_i$ , but not  $a_i$
- Concatenate
- Add lookup table (constant equation per bit)



- Consider S-box as lookup table with  $2^n$  entries (x, y)
- A correct circuit works for all possible values
- Create 2<sup>n</sup> copies of equations Note: unfortunately this encoding grows exponentially
- Rename  $x_i$ ,  $y_i$ ,  $q_i$ ,  $t_i$ , but not  $a_i$
- Concatenate
- Add lookup table (constant equation per bit)



Not bound to specific S-box yet

- Consider S-box as lookup table with  $2^n$  entries (x, y)
- A correct circuit works for all possible values
- Create 2<sup>n</sup> copies of equations Note: unfortunately this encoding grows exponentially
- Rename  $x_i$ ,  $y_i$ ,  $q_i$ ,  $t_i$ , but not  $a_i$
- Concatenate
- Add lookup table (constant equation per bit)

These equations are in ANF, but SAT solvers require CNF

Use method by Bard et al. for converting sparse systems of low-degree multivariate polynomials  $[{\sf BCJ07}]$ 



## Multiplicative complexity results

S-box	Size <i>n</i> × <i>m</i>	Multiplicative complexity
Ascon	5x5	5
ICEPOLE	5×5	6
Keccak/Ketje/Keyak	5×5	5
PRIMATEs	5×5	$\in \{6,7\}$
PRIMATEs <sup>-1</sup>	5×5	$\in \{6,7,8,9,10\}$
Joltik/Piccolo	4x4	4
Joltik <sup>-1</sup> /Piccolo <sup>-1</sup>	4x4	4
LAC	4x4	4
Minalpher	4x4	5
Prøst	4x4	4
RECTANGLE	4×4	4
RECTANGLE <sup>-1</sup>	4×4	4



Given a function f and some positive integer k, is there a circuit with only gates  $\in$  {AND, OR, XOR, NOT} that implements f and that uses at most k gates?



Given a function f and some positive integer k, is there a circuit with only gates  $\in \{AND, OR, XOR, NOT\}$  that implements f and that uses at most k gates?

#### Idea

Hard-code k gates of unknown type:

• Let *b<sub>i</sub>* be variables representing wiring *inside* gates



Given a function f and some positive integer k, is there a circuit with only gates  $\in \{AND, OR, XOR, NOT\}$  that implements f and that uses at most k gates?

#### Idea

Hard-code k gates of unknown type:

- Let *b<sub>i</sub>* be variables representing wiring *inside* gates
- $t_0 = b_0 \cdot q_0 \cdot q_1 + b_1 \cdot q_0 + b_1 \cdot q_1 + b_2 + b_2 \cdot q_0$   $0 = b_0 \cdot b_2$  $0 = b_1 \cdot b_2$



Given a function f and some positive integer k, is there a circuit with only gates  $\in \{AND, OR, XOR, NOT\}$  that implements f and that uses at most k gates?

#### Idea

Hard-code k gates of unknown type:

- Let *b<sub>i</sub>* be variables representing wiring *inside* gates
- $t_0 = b_0 \cdot q_0 \cdot q_1 + b_1 \cdot q_0 + b_1 \cdot q_1 + b_2 + b_2 \cdot q_0$   $0 = b_0 \cdot b_2$  $0 = b_1 \cdot b_2$



Given a function f and some positive integer k, is there a circuit with only gates  $\in$  {AND, OR, XOR, NOT} that implements f and that uses at most k gates?

#### Idea

Hard-code k gates of unknown type:

- Let *b<sub>i</sub>* be variables representing wiring *inside* gates
- $t_0 = b_0 \cdot q_0 \cdot q_1 + b_1 \cdot q_0 + b_1 \cdot q_1 + b_2 + b_2 \cdot q_0$   $0 = b_0 \cdot b_2$  $0 = b_1 \cdot b_2$

Gate input  $q_i$  can be precisely one:

- S-box input bit
- Previous gate output bit

Linear combination with additional at-most-1 constraints



## Bitslice gate complexity results

S-box	Bitslice gate complexity	Implementation		
Keccak/Ketje/Keyak	$\leq$ 13	3 AND, 2 OR, 5 XOR, 3 NOT		
Joltik/Piccolo	10	1 AND, 3 OR, 4 XOR, 2 NOT		
Joltik <sup>-1</sup> /Piccolo <sup>-1</sup>	10	1 AND, 3 OR, 4 XOR, 2 NOT		
LAC	11	2 AND, 2 OR, 6 XOR, 1 NOT		
Minalpher	$\geq 11$			
Prøst	8	4 AND, 4 XOR		
RECTANGLE	$\in \{11, 12\}$	1 AND, 3 OR, 7 XOR, 1 NOT		
RECTANGLE <sup>-1</sup>	$\in \{10, 11, 12\}$	4 OR, 7 XOR, 1 NOT		



# Gate complexity

Only difference:  $t_0 = b_0 \cdot q_0 \cdot q_1 + b_1 \cdot q_0 + b_1 \cdot q_1 + b_2$ 

$b_{3i}b_{3i+1}b_{3i+2}$	Gate $t_i$ function
000	0
001	1
010	$q_{2i}\oplus q_{2i+1}$
011	$q_{2i} \leftrightarrow q_{2i+1}$
100	$q_{2i} \wedge q_{2i+1}$
101	$q_{2i} \uparrow q_{2i+1}$
110	$q_{2i} \lor q_{2i+1}$
111	$q_{2i}\downarrow q_{2i+1}$





## Gate complexity results

S-box	Gate complexity	Implementation		
Joltik/Piccolo	8	2 OR, 1 XOR, 2 NOR, 3 XNOR		
Joltik <sup>-1</sup> /Piccolo <sup>-1</sup>	8	2 OR, 1 XOR, 2 NOR, 3 XNOR		
LAC	10	1 AND, 3 OR, 2 XOR, 4 XNOR		
Prøst	8	4 AND, 4 XOR		
RECTANGLE	$\in \{10,11\}$	1 AND, 1 OR, 2 XOR, 1 NAND,		
		1 NOR, 5 XNOR		
RECTANGLE <sup>-1</sup>	$\in \{10,11\}$	1 AND, 1 OR, 6 XOR, 1 NAND,		
		1 NOR, 1 XNOR		





# Circuit depth complexity

Decreasing the depth of a circuit allows for increasing the clock frequency





## Circuit depth complexity

Decreasing the depth of a circuit allows for increasing the clock frequency

Every function can be implemented in depth 2 (normal forms) However, at the cost of more gates (width)





## Circuit depth complexity

Decreasing the depth of a circuit allows for increasing the clock frequency

Every function can be implemented in depth 2 (normal forms) However, at the cost of more gates (width)

#### Idea

Introduce maximum width w

Given a function f and some positive integer k, is there a circuit of depth at most k and width at most w that implements f?

Encoding like gate complexity, but gate input  $q_i$  is now either S-box input or gate output on previous depth layer



## Circuit depth complexity results

S-box	k	W	Implementation	UNSAT bounds
Joltik/Piccolo	4	2	2 OR, 1 XOR,	k = 4, w = 1
			2 NOR, 3 XNOR	k = 3, w = 10
Joltik <sup>-1</sup> /Piccolo <sup>-1</sup>	4	3	3 OR, 5 XOR,	k = 4, w = 2
			1 NOR, 3 XNOR	k = 3, w = 10
LAC	3	6	3 OR, 4 XOR,	k = 3, w = 4
			4 NAND, 4 XNOR	k = 2, w = 10
Prøst	4	3	4 AND, 1 OR, 4 XOR,	k = 4, w = 2
			1 NAND, 1 XNOR	k = 3, w = 10
RECTANGLE	3	6	2 AND, 3 OR, 5 XOR,	k = 3, w = 4
			1 NAND, 1 NOR, 3 XNOR	k = 2, w = 10
RECTANGLE <sup>-1</sup>	3	6	1 OR, 8 XOR,	k = 3, w = 4
			3 NAND, 2 NOR, 2 XNOR	k = 2, w = 10



# Combining criteria

What about combinations?



# Combining criteria

What about combinations?

Lets optimize PRIMATEs 5x5 S-box

- First for multiplicative complexity
- Then reduce linear gates, i.e. XOR, NOT



# Combining criteria

What about combinations?

Lets optimize PRIMATEs 5x5 S-box

- First for multiplicative complexity
- Then reduce linear gates, i.e. XOR, NOT

Apply existing methods for solving the Shortest Linear Straight-Line Program (SLP) problem

- Exact, using SAT solvers (Fuhs-Schneider-Kamp [FSK10])
- Heuristics (Boyar–Peralta [BP10])



#### SLP

Given  $\mathbb{F}$  and constants  $a_{i,j} \in \mathbb{F}$ , compute linear forms

$$a_{1,1}x_1 + a_{1,2}x_2 + \dots + a_{1,n}x_n$$
  

$$a_{2,1}x_1 + a_{2,2}x_2 + \dots + a_{2,n}x_n$$
  

$$\dots$$
  

$$a_{m,1}x_1 + a_{m,2}x_2 + \dots + a_{m,n}x_n$$

in the shortest number of program lines of the form

 $u := \lambda v + \mu w$ 

where  $\lambda,\mu\in\mathbb{F}$ 



$a = x_0 \oplus x_0$	$a_{2} - x_{2} \oplus t_{2} \oplus t_{3}$
$q_0 = x_0 \oplus x_3$	$q_9 = x_2 \oplus t_0 \oplus t_3$
$q_1 = x_1$	$t_4=q_8\wedge q_9$
$\mathit{t_0} = \mathit{q_0} \lor \mathit{q_1}$	$q_{10} = x_0 \oplus x_3 \oplus x_4$
$q_2 = \neg(x_1 \oplus x_3)$	$q_{11} = \neg(x_0 \oplus x_4)$
$q_3 = x_0 \oplus x_2$	$t_5=q_{10}\vee q_{11}$
$t_1=q_2\wedge q_3$	$q_{12} = \neg (x_1 \oplus x_2 \oplus t_0 \oplus t_2 \oplus t_3 \oplus t_4)$
$q_4 = x_0 \oplus x_1 \oplus x_4$	$q_{13} = x_2 \oplus x_3$
$q_5 = x_0 \oplus x_2 \oplus x_3$	$t_6=q_{12}\wedge q_{13}$
$t_2=q_4\wedge q_5$	$y_0 = x_1 \oplus x_3 \oplus t_2 \oplus t_3 \oplus t_5 \oplus t_6$
$q_6 = \neg (x_0 \oplus x_2 \oplus x_3 \oplus x_4)$	$y_1 = x_0 \oplus x_4 \oplus t_1 \oplus t_2 \oplus t_3 \oplus t_4 \oplus t_5 \oplus t_6$
$q_7 = x_1 \oplus x_2 \oplus x_4$	$y_2 = x_1 \oplus x_2 \oplus x_4 \oplus t_1 \oplus t_3 \oplus t_4 \oplus t_5$
$t_3=q_6 \lor q_7$	$y_3 = x_0 \oplus x_2 \oplus x_3 \oplus x_4 \oplus t_3 \oplus t_4 \oplus t_5 \oplus t_6$
$q_8 = x_0 \oplus x_1 \oplus x_2 \oplus x_3 \oplus x_4$	$y_4 = \neg (x_2 \oplus t_0 \oplus t_2 \oplus t_3 \oplus t_4 \oplus t_5 \oplus t_6)$



• Treat linear operations before and after nonlinear operations as two separate SLP instances



- Treat linear operations before and after nonlinear operations as two separate SLP instances
- Try exact method



- Treat linear operations before and after nonlinear operations as two separate SLP instances
- Try exact method
- If infeasible, try heuristic method





- Treat linear operations before and after nonlinear operations as two separate SLP instances
- Try exact method
- If infeasible, try heuristic method





- Treat linear operations before and after nonlinear operations as two separate SLP instances
- Try exact method
- If infeasible, try heuristic method

Managed to reduce 58 XOR gates to 31 XOR gates



$z_0 = x_0 \oplus x_4$	$q_7 = x_4 \oplus z_1$	$z_5 = t_2 \oplus z_4$
$z_1 = x_1 \oplus x_2$	$t_3=q_6\vee q_7$	$z_6 = t_1 \oplus t_6$
$z_2 = x_2 \oplus x_3$	$q_8=q_4\oplus z_2$	$z_7 = t_4 \oplus z_5$
$q_0 = x_0 \oplus x_3$	$z_9 = t_0 \oplus t_3$	$z_8 = t_1 \oplus z_7$
$t_0 = q_0 \vee x_1$	$q_9=x_2\oplus z_9$	$z_{10} = t_0 \oplus z_7$
$q_2 = x_1 \oplus x_3$	$t_4=q_8\wedge q_9$	$z_{11} = t_4 \oplus z_4$
$q_3 = \neg(x_0 \oplus x_2)$	$q_{10} = \neg(x_3 \oplus z_0)$	$z_{12}=z_6\oplus z_{11}$
$t_1 = q_2 \vee q_3$	$t_5=q_{10}\wedge z_0$	$y_0 = \neg(q_2 \oplus z_5)$
$q_4 = x_1 \oplus z_0$	$q_{12}=\neg(z_1\oplus z_9\oplus t_2\oplus t_4)$	$y_1 = z_0 \oplus z_8$
$q_5 = x_0 \oplus z_2$	$t_6=q_{12}\wedge z_2$	$y_2 = q_7 \oplus z_{12}$
$t_2 = q_4 \wedge q_5$	$z_3 = t_5 \oplus t_6$	$y_3 = q_6 \oplus z_{11}$
$q_6 = \neg(x_4 \oplus q_5)$	$z_4 = t_3 \oplus z_3$	$y_4 = x_2 \oplus z_{10}$



• The paper includes all optimized implementations in the appendix



- The paper includes all optimized implementations in the appendix
- Tools to automate this (generate equations, convert to CNF, solve, retrieve result and corresponding implementation) are available online and in the public domain

https://ko.stoffelen.nl/





- The paper includes all optimized implementations in the appendix
- Tools to automate this (generate equations, convert to CNF, solve, retrieve result and corresponding implementation) are available online and in the public domain

https://ko.stoffelen.nl/

• For small functions, our method works quite nicely



- The paper includes all optimized implementations in the appendix
- Tools to automate this (generate equations, convert to CNF, solve, retrieve result and corresponding implementation) are available online and in the public domain

https://ko.stoffelen.nl/

- For small functions, our method works quite nicely
- Not feasible for, say, 8-bit S-boxes because of exponential encoding E.g., RECTANGLE with k = 5, w = 4 already has 21372 variables and 106151 clauses in CNF



- The paper includes all optimized implementations in the appendix
- Tools to automate this (generate equations, convert to CNF, solve, retrieve result and corresponding implementation) are available online and in the public domain

https://ko.stoffelen.nl/

- For small functions, our method works quite nicely
- Not feasible for, say, 8-bit S-boxes because of exponential encoding E.g., RECTANGLE with k = 5, w = 4 already has 21372 variables and 106151 clauses in CNF
- Thanks for your attention





#### **References** I

Gregory V. Bard, Nicolas T. Courtois, and Chris Jefferson. Efficient methods for conversion and solution of sparse systems of low-degree multivariate polynomials over GF(2) via SAT-solvers. Cryptology ePrint Archive, Report 2007/024, 2007. http://eprint.iacr.org/.

#### Joan Boyar and René Peralta.

A new combinational logic minimization technique with applications to cryptology. In Paola Festa, editor, *Experimental Algorithms*, volume 6049 of *Lecture Notes in Computer Science*, pages 178–189. Springer Berlin Heidelberg, 2010.



#### Nicolas Courtois, Theodosis Mourouzis, and Daniel Hulme.

Exact logic minimization and multiplicative complexity of concrete algebraic and cryptographic circuits.

International Journal On Advances in Intelligent Systems, 6(3 and 4):165-176, 2013.



#### Carsten Fuhs and Peter Schneider-Kamp.

#### Synthesizing shortest linear straight-line programs over GF(2) using SAT.

In Ofer Strichman and Stefan Szeider, editors, *Theory and Applications of Satisfiability Testing – SAT 2010*, volume 6175 of *Lecture Notes in Computer Science*, pages 71–84. Springer Berlin Heidelberg, 2010.





#### References II



Theodosis Mourouzis.

**Optimizations in Algebraic and Differential Cryptanalysis.** PhD thesis, UCL (University College London), 2015.

